


Name: _____




The Blobz Guide to Electric Circuits

<http://www.andythelwell.com/blobz/>

 Draw a complete circuit in the first box.



 Draw an incomplete circuit in the second box.



Name two conductors: _____

What do switches allow you to do? _____

What might happen if you add too many cells to a circuit? _____
